

# CSC258: Computer Organization

Instructors: Steve Engels, [sengels@cs.toronto.edu](mailto:sengels@cs.toronto.edu)  
Chandra Gummalluru, [chandra@cs.toronto.edu](mailto:chandra@cs.toronto.edu)

1

## What we're covering today

- A little about us
- What CSC258 is about
- What CSC258 involves
- Course outcomes
- Next steps



2

What is CSC258 about?



4

Maximum integer value:  $2^{32} - 1$   
How does your computer work?

- To understand computer software, you need to understand computer hardware.

## Limitations

Why is the maximum integer value  $2^{32}-1$ ?

## Operations

## What is a pointer? How is memory allocated?

## Behaviour

### What is a stack overflow? How do exceptions work? What causes a blue screen error?

5

## Example: True and False

- How does Python evaluate true and false?

- Example: if statements:

```
if x:
    print 'Hello World'
# what values of x will make this
# print statement happen?
```

- What if x is a Boolean?
  - What if x is an integer?
  - What if x is a string?
- } Do the answers to these questions have something in common?

6

## True and False in Python

- Values that are treated as "false":

- Constants defined to be "false":
  - None and False.
- Numeric zero values:
  - 0, 0.0, Decimal(0), Fraction(0,1)
- Empty sequences and collections:
  - '', (), [], {}, set(), range(0)

"By default, an object is considered true unless its class defines either a `__bool__()` method that returns False or a `__len__()` method that returns zero, when called with the object."

<https://docs.python.org/3/library/stdtypes.html#truth-value-testing>

- What do these "false" values have in common?

- They're all represented the same way in memory.
  - i.e. Zero vs not zero
- One of the many things you learn in CSC258 ☺


7

## Why are you taking CSC258?


### Understanding the machine



### Satisfying prerequisites

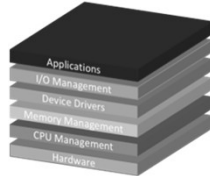

### Working with devices (IoT)

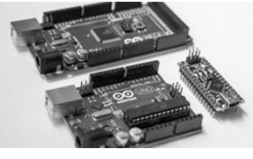


### Because you have to



I know what I have to do but I don't know if I have the strength to do it.


8

## How the course works

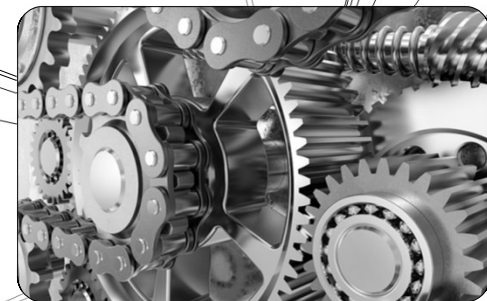


9

## The course at a glance

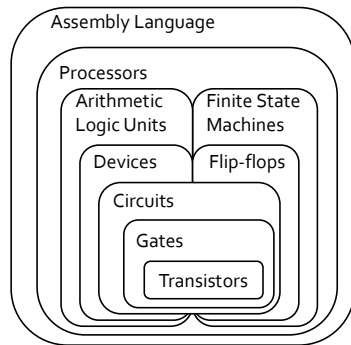

10

## Lectures & Tutorials

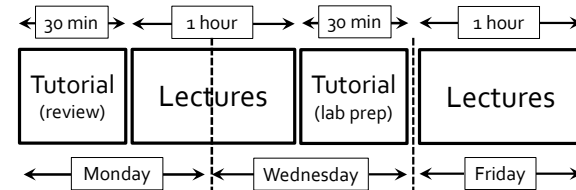


- Lectures (2 hours total)
  - Lectures cover course topics (generally one per week)
  - Each week builds on the week before
  - 2022 recordings will be available on Quercus
- Tutorials
  - Monday: 30 minutes topic review (from previous week)
  - Wednesday: 30 minutes lab prep (for following week)

11
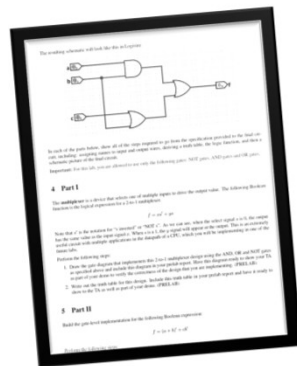
## Lab Exercises

- Labs (28%):
  - 7 total (4% each)
    - One lab per week, starting in Week 2 (week of Sept 8<sup>th</sup>)
  - Each lab consists of two parts:
    - **Pre-lab** → 1%
      - Circuit creation exercises
      - Submit on Quercus before lab
    - **Demo** → 3%
      - Performed for TAs in labs
      - Minimum standard questions



13

## How do the labs work?

- Everybody has 3 hours of lecture time and a 3-hour lab time assigned to this course.
  - L0101 lab time: Tuesdays, 6pm-9pm
  - L0201 lab time: Wednesdays, 6pm-9pm
  - L5101 lab time: Thursdays, 6pm-9pm
- Students attend their lab session and sit at their designated station (assigned during the first lab in Week 2)
  - Pre-labs exercises are submitted before the lab,
  - Completed work is demonstrated during the lab session.
- Labs take place in BA3145, BA3155 and BA3165.
  - Students are assigned to a lab room according to last name (see Quercus to know which room you're in).

14

## Project

### ■ Assembly Language Project (15%):

- Create an interactive game in MIPS assembly.
- 5 cumulative milestones (3% each)
  - Milestones 1-3: Basic game features
  - Milestones 4-5: Advanced features
  - Can demo all 5 in the first week, if you want.
- Milestone demos take place in the lab rooms with the TAs in the final two weeks of the course.
  - Including questions about the design process.



15

## Midterm & Final Exam

### ■ Midterm (19%)

- Tentatively scheduled for **Thurs Oct 16, 6pm-8pm**
- If you have a conflict with an existing class or lab, contact the course email account by Oct 1, along with your course schedule.

### ■ Final Exam (38%)

- In-person assessment (3 hours to write)
- **You must get 40% on the exam to pass the course.**
- Exam date will be released midway through the semester.

16

## Course Objectives



17

## Course outcomes


*Circuits from logic gates*

- Circuit creation
  - Create combinational and sequential circuits from logic gates.
  - Design circuits that implement Finite State Machines
- Microprocessor architecture
  - Implement a basic arithmetic logic unit (ALU)
  - Develop register files and memory units
  - Construct and operate the processor datapath.
- Assembly basics
  - Encode and decode microprocessor instructions
  - Translate between assembly and C programs

18
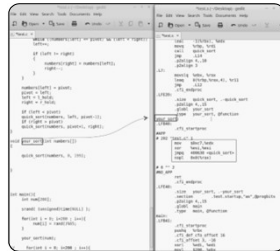
## Building on CSC148

- Hardware knowledge helps us make sense of the software knowledge from CSC148.
  - Think of CSC258 as the prequel to CSC108 and CSC148 (or CSC110 & CSC111)
- CSC258 also complements the material in CSC209.
  - Helps you understand pointers and memory operations.



19

## Building on CSC165 / CSC110

- Logic notation and reasoning is essential in the beginning of the course.
- In CSC165 (or CSC110) you use propositional logic to evaluate statements to be true or false.
- In CSC258 you create circuits whose output value evaluates to true or false, based on the input values.
  - Electrical equivalent of "true" and "false" are high voltage (5 V) and low voltage (-5 V).
  - Also known as binary bits 1 and 0, which we see soon.

20


## Connecting to intro courses

- From CSC165: Create an expression  $G$  that is true if the variables  $A$  and  $B$  are true, or  $C$  and  $D$  are true.


$$G = (A \wedge B) \vee (C \wedge D)$$

*Handwritten notes: "True" above the first AND, "False" above the second AND, "True" above the OR.*

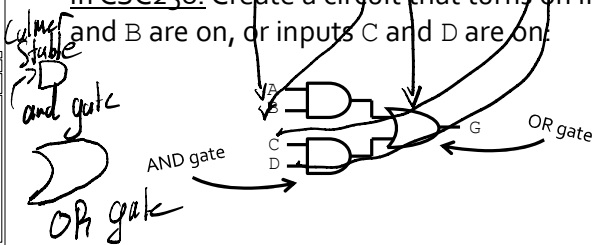- In CSC258: Create a circuit that turns on if inputs  $A$  and  $B$  are on, or inputs  $C$  and  $D$  are on.




21

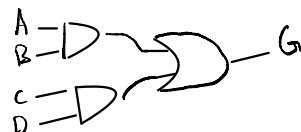
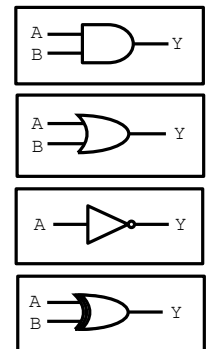
## Logic Gates ↔ Operators



- Logic gates are the hardware equivalent of propositional operators in CSC165/CSC110.
  - Like Boolean expressions, gates determine whether the output of a circuit will be on or off as an expression of the input signals.
- Lab 1:
  - Create simple circuits based on logical (Boolean) expressions
  - Display truth tables that show the logical behaviour of these circuits.



22
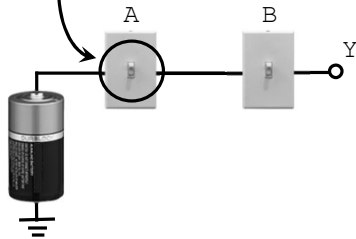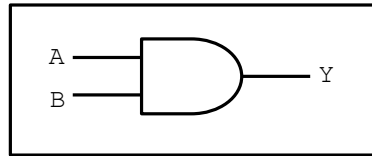
## AND Gates

These are implemented by components called transistors. We'll learn about them shortly. For now, think of them like switches that connect the left and right when A is turned on.




A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

23


## OR Gates

NOT Gates

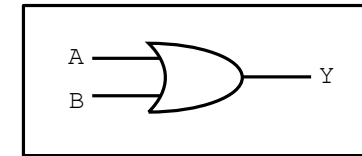

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


## NOT Gates

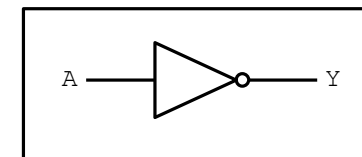

A	Y
0	1
1	0


24

## XOR Gates

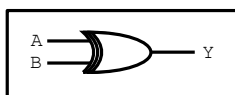


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

## NAND Gates

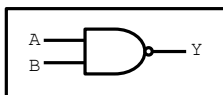

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


## NOR Gates

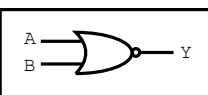


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

25

## Buffer

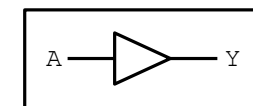


A	Y
0	0
1	1

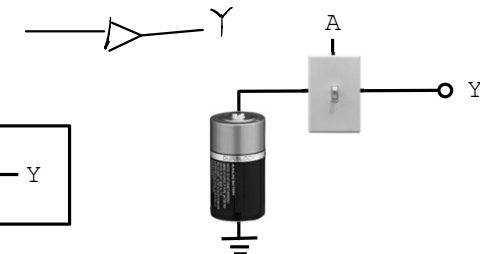

- ...more in Week 9 about what makes this gate useful.

26

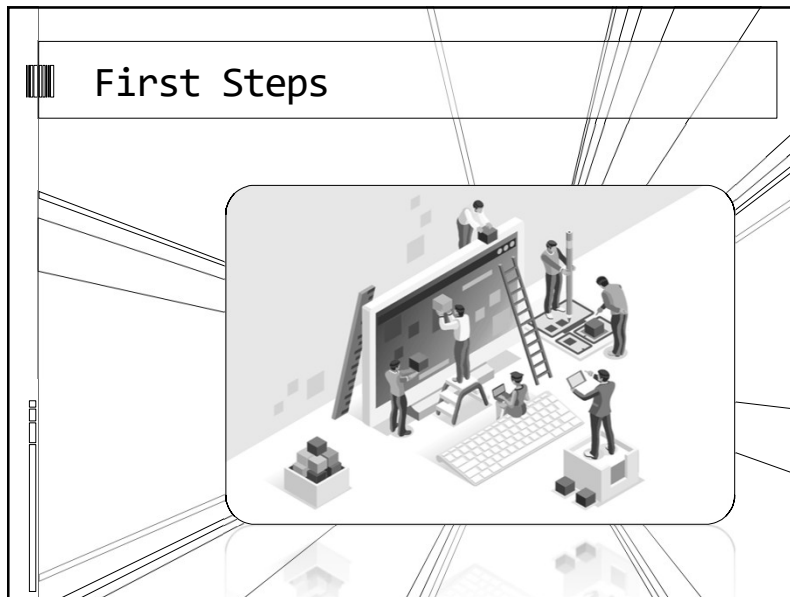

27

## Thinking in hardware

*Very important concept*


- Although CSC258 has elements that are similar to other courses, it is very different in significant ways.
  - Unlike our software courses, CSC258 is not about creating programs and algorithms, but rather devices and machines.
  - Very important concept to grasp early in this course!

28

## Starting from the bottom

- Gates can combine values together like logical operators in C or Java.
- But how do gates work?
  - First, we need to understand electricity.
  - Then, we need to understand transistors.
  - Finally, transistors are combined to create logic gates.

29

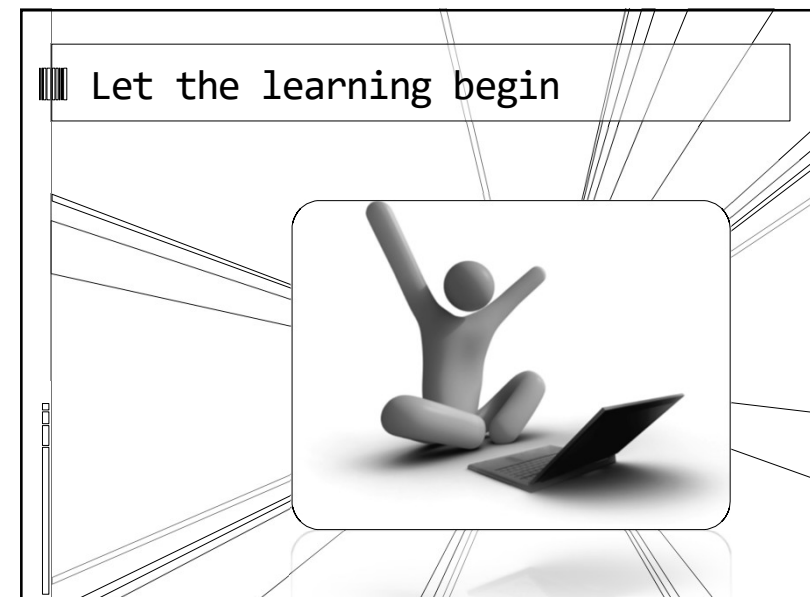

30